

1. JK Flip-flop :

VHDL module :

```
--libraries to be used are specified here
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity JK_Flipflop is
port ( clk:          in std_logic;
      J, K:          in std_logic;
      Q, Qbar:       out std_logic;
      reset:         in std_logic
);
end JK_Flipflop;
--architecture of entity
architecture Behavioral of JK_Flipflop is
--signal declaration.
signal qtemp: std_logic := '0';
signal qbartemp: std_logic := '1';
begin
Q <= qtemp;
Qbar <= qbartemp;
process(clk,reset)
begin
if(reset = '1') then
qtemp <= '0';
qbartemp <= '1';
elsif( rising_edge(clk) ) then
if(J='0' and K='0') then
NULL;
elsif(J='0' and K='1') then
qtemp <= '0';
qbartemp <= '1';
elsif(J='1' and K='0') then
qtemp <= '1';
qbartemp <= '0';
else
qtemp <= not qtemp;
qbartemp <= not qbartemp;
end if;
end if;
end process;
end Behavioral;
```

Testbench :

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity JK_Flipflop_tb is
end JK_Flipflop_tb;
architecture behavior of JK_Flipflop_tb is
--Signal declarations
component JK_Flipflop
port ( clk:          in std_logic;
      J, K:          in std_logic;
```

```

        Q, Qbar:   out std_logic;
        reset:    in std_logic
    );
end component;
signal clk,J,K,reset,Q,Qbar : std_logic := '0';
-- Clock period definitions
constant clk_period : time := 100 ns;
shared variable simend : boolean := false;
begin
-- Instantiate the Unit Under Test (UUT)
UUT : JK_Flipflop port map (clk,J,K,Q,Qbar,reset);
-- Clock process definitions
clk_process :process
begin
    while simend=false loop
        clk <= not clk;
        wait for clk_period/2;
    end loop;
    wait;
end process;
-- Stimulus process
stim_proc: process
begin
    J<='0';
    K<='0';
    wait for clk_period*2;
    J<='1';
    K<='0';
    wait for clk_period*2;
    J<='1';
    K<='1';
    wait for clk_period*2;
    J<='0';
    K<='1';
    wait for clk_period*2;
    J<='0';
    K<='0';
    wait for clk_period*2;

    J<='1';
    K<='0';
    wait for clk_period*2;
    reset <='1';
    J<='1';
    K<='1';
    wait for clk_period*2;
    J<='0';
    K<='1';
    wait for clk_period*2;
    reset <='0';
    J<='1';
    K<='1';


```

```

simend := true;
wait;
end process;
end;

```

WAVEFROM :

 

2. T Flip-flop :

VHDL module :

```

library ieee;
use ieee.std_logic_1164.all;
entity TFF is
port( din: in std_logic;
      clk: in std_logic;
      rst: in std_logic;
      dout: out std_logic);
end TFF;
architecture behavioral of TFF is
begin
process(rst,clk,din)
begin
if (rst='1') then
dout<='0';
elsif(rising_edge(clk)) then
dout<=not din;
end if;
end process;
end behavioral;

```

Testbench:

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY TFF_tb IS
END TFF_tb;
  COMPONENT TFF
  PORT(
    din : IN std_logic;
    clk : IN std_logic;
    rst : IN std_logic;
    dout : OUT std_logic

```

```

    );
END COMPONENT;

signal din : std_logic := '0';
signal clk : std_logic := '0';
signal rst : std_logic := '0';
signal dout : std_logic;

constant clk_period : time := 10 ns;

BEGIN

    uut: TFF PORT MAP (
        din => din,
        clk => clk,
        rst => rst,
        dout => dout
    );

    clk_process : process
    begin
        clk <= '0';
        wait for clk_period/2;
        clk <= '1';
        wait for clk_period/2;
    end process;

    stim_proc: process
    begin


        rst <= '1';
        wait for 50 ns;

        rst <= '0';
        din <= '0';
        wait for 50 ns;

        rst <= '0';
        din <= '1';
        wait;
    end process;
END;

```

WAVEFROM :

 

3. D-Flip-flop :

VHDL module :

```
library ieee;
use ieee.std_logic_1164.all;
entity dff is
    port(CLK, RESET, D : in std_logic;
          Q : out std_logic);
end dff;
architecture pet_pr of dff is

begin
    process (CLK, RESET)
    begin
        if (RESET = '1') then
            Q <= '0';
        elsif (CLK'event and CLK = '1') then
            Q <= D;
        end if;
    end process;
end;
```

Testbench :

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity DFF_tb is
end DFF_tb;
architecture behavior of DFF_tb is
--Signal declarations
    component DFF
    port(CLK, RESET, D : in std_logic;
          Q : out std_logic);
    end component;

    signal clk,reset, d, q: std_logic := '0';
    constant clk_period : time := 100 ns;
    shared variable simend : boolean := false;

begin
    -- Instantiate the Unit Under Test (UUT)
    UUT :DFF port map (clk => CLK,reset => RESET, d => D, q => Q);
    -- Clock process definitions
    clk_process :process
    begin
        while simend=false loop
            clk <= not clk;
```

```

        wait for clk_period/2;
    end loop;
    wait;
end process;
-- Stimulus process
stim_proc: process
begin
    D <='0';
    wait for clk_period*2;

    D <='1';
    wait for clk_period*2;

    reset <='1';
    D <='0';
    wait for clk_period*2


    D <='1';
    wait for clk_period*2;

    simend := true;

    wait;
end process;
end;

```

WAVEFROM :

 

4. 4-Bit Register :

VHDL module :

```

library ieee;
use ieee.std_logic_1164.all;

entity dff is
    port(
        clk, reset, d : in std_logic;
        q : out std_logic
    );

```

```

end dff;

architecture behavioral_dff of dff is
begin
    process (clk, reset)
    begin
        if (reset = '1') then
            q <= '0';
        elsif (clk'event and clk = '1') then
            q <= d;
        end if;
    end process;
end behavioral_dff;

library ieee;
use ieee.std_logic_1164.all;

entity reg is
    port (
        d: in std_logic_vector(3 downto 0);
        clk, clear: in std_logic;
        q: out std_logic_vector(3 downto 0)
    );
end reg;

architecture behavioral_reg of reg is
    component dff
        port(
            clk, reset, d : in std_logic;
            q : out std_logic
        );
    end component;

    signal reset: std_logic:= '0';

begin
    dff0: dff
    port map (clk, reset, d(0), q(0));
    dff1: dff
    port map (clk, reset, d(1), q(1));
    dff2: dff
    port map (clk, reset, d(2), q(2));
    dff3: dff
    port map (clk, reset, d(3), q(3));

end behavioral_reg;

```

Testbench:

```

library ieee;

```

```

use ieee.std_logic_1164.all;

entity reg_tb is
end reg_tb;

architecture behavioral_reg_tb of reg_tb is
    component reg
        port(
            d: in std_logic_vector(3 downto 0);
            clk, clear: in std_logic;
            q: out std_logic_vector(3 downto 0)
        );
    end component;

    signal d, q: std_logic_vector(3 downto 0);
    signal clk, clear: std_logic := '0';

    constant clk_period : time := 100 ns;
    shared variable simend : boolean := false;

begin
    uut : reg port map (clk => clk, clear => clear, d => d, q => q);

    clk_process : process
    begin
        while simend=false loop
            clk <= not clk;
            wait for clk_period/2;
        end loop;
        wait;
    end process;

    stim_proc: process
    begin
        d(0) <= '0'; d(1) <= '0'; d(2) <= '0'; d(3) <= '0';
        wait for clk_period*2;

        d(0) <= '0'; d(1) <= '1'; d(2) <= '0'; d(3) <= '1';
        wait for clk_period*2;


        clear <= '1';
        d(0) <= '1'; d(1) <= '0'; d(2) <= '1'; d(3) <= '1';
        wait for clk_period*2;

        d(0) <= '0'; d(1) <= '0'; d(2) <= '1'; d(3) <= '1';
        wait for clk_period*2;
        simend := true;

        wait;
    end process;
end behavioral_reg_tb;

```


WAVEFROM :

 

5. 4-Bit Counter :

VHDL module :

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity UPDOWN_COUNTER is
    Port ( clk: in std_logic; -- clock input
          reset: in std_logic; -- reset input
          up_down: in std_logic; -- up or down
          counter: out std_logic_vector(3 downto 0) -- output 4-bit counter
    );
end UPDOWN_COUNTER;
```

```
architecture Behavioral of UPDOWN_COUNTER is
    signal counter_updown: std_logic_vector(3 downto 0);
begin
    process(clk,reset)
    begin
        if(rising_edge(clk)) then
            if(reset='1') then
                counter_updown <= x"0";
            elsif(up_down='1') then
                counter_updown <= counter_updown - x"1"; -- count down
            else
                counter_updown <= counter_updown + x"1"; -- count up
            end if;
        end if;
    end process;
    counter <= counter_updown;
end Behavioral;
```

Testbench :

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity tb_counters is
end tb_counters;

architecture Behavioral of tb_counters is
    component UPDOWN_COUNTER
```

```


Port ( clk: in std_logic; -- clock input
      reset: in std_logic; -- reset input
      up_down: in std_logic;
      counter: out std_logic_vector(3 downto 0) -- output 4-bit counter
    );
end component;
signal reset,clk,up_down: std_logic;
signal counter:std_logic_vector(3 downto 0);

begin
dut: UPDOWN_COUNTER port map (clk=> clk, reset=>reset, up_down => up_down, counter => counter);

clock_process :process
begin
    clk <= '0';
    wait for 10 ns;
    clk <= '1';
    wait for 10 ns;
end process;
stim_proc: process
begin
    reset <= '1';
    up_down <= '0';
    wait for 20 ns;
    reset <= '0';
    wait for 300 ns;
    up_down <= '1';
    wait;
end process;
end Behavioral;

```

Waveform :

 

6. 4-Bit Shift Register :

VHDL module :

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity shiftreg_4bit is
    Port ( Din : in STD_LOGIC;
          CLK : in STD_LOGIC;

```

```

        RESET : in STD_LOGIC;
        Q : out STD_LOGIC_VECTOR (3 downto 0));
end shiftreg_4bit;

architecture Structural of shiftreg_4bit is component DF is
    Port ( D : in STD_LOGIC;
          CLK : in STD_LOGIC;
          RESET : in STD_LOGIC;
          Q : out STD_LOGIC);
    end component;
signal Qtemp : STD_LOGIC_VECTOR (3 downto 1);
begin
    DF3 : DF port map (Din, CLK, RESET, Qtemp(3));
    DF2 : DF port map (Qtemp(3), CLK, RESET, Qtemp(2));
    DF1 : DF port map (Qtemp(2), CLK, RESET, Qtemp(1));
    DF0 : DF port map (Qtemp(1), CLK, RESET, Q(0));

    Q(3 downto 1) <= Qtemp;
end Structural;

```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

```

entity DF is
    Port ( D : in STD_LOGIC;
          CLK : in STD_LOGIC;
          RESET: in STD_LOGIC;
          Q : out STD_LOGIC);
end DF;
architecture Behavioral of DF is

```

```

begin
    process (CLK, RESET)
    begin
        if(RESET = '1') then
            Q <= '0';
        elsif(rising_edge(CLK)) then
            Q <= D;
        end if;
    end process;
end Behavioral;

```

Test bench :

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY tb_shiftreg_4bit IS
END tb_shiftreg_4bit;

```

```

ARCHITECTURE behavior OF tb_shiftreg_4bit IS

```

```

    COMPONENT shiftreg_4bit

```

```

PORT(
    Din : IN std_logic;
    CLK : IN std_logic;
    RESET : IN std_logic;
    Q : OUT std_logic_vector(3 downto 0)
);
END COMPONENT;
signal Din : std_logic := '0';
signal CLK : std_logic := '0';
signal RESET : std_logic := '0';
signal Q : std_logic_vector(3 downto 0);
BEGIN
    uut: shiftreg_4bit PORT MAP (
        Din => Din,
        CLK => CLK,
        RESET => RESET,
        Q => Q
    );
    CLK_process :process
    begin
        CLK <= '0';
        wait for 100 ns;
        CLK <= '1';
        wait for 100 ns;

    end process;
    stim_proc: process
    begin

        RESET <= '1';
        Din <= '1';
        wait for 200 ns;
        Reset <= '0';

    end process;
END

```

Wavefrom :

