

D-FlipFlop:

VHDL Module:

```
library ieee;
use ieee.std_logic_1164.all;
entity d is
port(
D : in std_logic;
CLK : in std_logic;
RESET : in std_logic;
Q : out std_logic);
end d;
architecture behavioral of d is
begin
process (CLK, RESET)
begin
if (RESET = '1') then
Q <= '0';
elsif (CLK'event and CLK = '1') then
Q <= D;
end if;
end process;
end;
```

VHDL TestBench:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity DFF_tb is
```

```

end DFF_tb;

architecture behavior of DFF_tb is

--Signal declarations

component DFF
port(CLK, RESET, D : in std_logic;
Q : out std_logic);
end component;

signal clk,reset, d, q: std_logic := '0';

-- Clock period definitions

constant clk_period : time := 100 ns;

shared variable simend : boolean := false;


begin

-- Instantiate the Unit Under Test (UUT)
UUT :DFF port map (clk => CLK,reset => RESET, d => D, q => Q);

-- Clock process definitions
clk_process :process
begin
while simend=false loop
clk <= not clk;

wait for clk_period/2;

end loop;

wait;

end process;

-- Stimulus process
stim_proc: process
begin

D <='0';

```

```
wait for clk_period*2;
```

```
D <='1';
```

```
wait for clk_period*2;
```

```
reset <='1';
```

```
D <='0';
```

```
wait for clk_period*2;
```

```
D <='1';
```

```
wait for clk_period*2;
```

```
simend := true;
```

```
wait;
```

```
end process;
```

```
end;
```

Output(D-flipflop):



Figure : Simulation output of D-flipflop

JK-Flipflop:

VHDL Module:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity JK_Flipflop is
port ( clk:      in std_logic;
      J, K:      in std_logic;
      Q, Qbar:   out std_logic;
      reset:     in std_logic
    );
end JK_Flipflop;

--architecture of entity
architecture Behavioral of JK_Flipflop is
--signal declaration.
signal qtemp: std_logic := '0';
signal qbartemp: std_logic := '1';
begin
  Q <= qtemp;
  Qbar <= qbartemp;
  process(clk,reset)
  begin
    if(reset = '1') then      --Reset the output.
      qtemp <= '0';
      qbartemp <= '1';
    elsif( rising_edge(clk) ) then
      if(J='0' and K='0') then  --No change in the output
        NULL;
      elsif(J='0' and K='1') then  --Reset the output.
```

```

qtemp <= '0';
qbartemp <= '1';
elsif(J='1' and K='0') then    --Set the output.
qtemp <= '1';
qbartemp <= '0';
else                            --Toggle the output.
qtemp <= not qtemp;
qbartemp <= not qbartemp;
end if;
end if;
end process;
end Behavioral;

```

VHDL Testbench:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity JK_Flipflop_tb is
end JK_Flipflop_tb;
architecture behavior of JK_Flipflop_tb is
--Signal declarations
component JK_Flipflop
port ( clk:      in std_logic;
J, K:      in std_logic;
Q, Qbar:  out std_logic;
reset:    in std_logic);
end component;
signal clk,J,K,reset,Q,Qbar : std_logic := '0';
-- Clock period definitions
constant clk_period : time := 100 ns;

```

```

shared variable simend : boolean := false;

begin
-- Instantiate the Unit Under Test (UUT)
UUT : JK_Flipflop port map (clk,J,K,Q,Qbar,reset);
-- Clock process definitions
clk_process :process
begin
while simend=false loop
clk <= not clk;
wait for clk_period/2;
end loop;
wait;
end process;
stim_proc: process
begin
J<='0';K<='0';
wait for clk_period*2;
J<='1';
K<='0';
wait for clk_period*2;
J<='1';
K<='1';
wait for clk_period*2;
J<='0';
K<='1';
wait for clk_period*2;

J<='0';

```

```
K<='0';  
wait for clk_period*2;  
J<='1';  
K<='0';  
wait for clk_period*2;  
reset <='1';  
J<='1';  
K<='1';  
wait for clk_period*2;  
J<='0';  
K<='1';  
wait for clk_period*2;  
reset <='0';  
J<='1';  
K<='1';  
simend := true;  
wait;  
end process;  
end;
```

Output(JK-flipflop)

 


Figure : Simulation output of JK flipflop

4-Bit Register:

VHDL Module:

```
library ieee;
use ieee.std_logic_1164.all;
entity dff is
port(
clk, reset, d : in std_logic;
q : out std_logic      );
end dff;
architecture behavioral_dff of dff is
begin
process (clk, reset)
begin
if (reset = '1') then
q <= '0';
elsif (clk'event and clk = '1') then
q <= d;
end if;
end process;
end behavioral_dff;

library ieee;
use ieee.std_logic_1164.all;
entity reg is
port (
d: in std_logic_vector(3 downto 0);
clk, clear: in std_logic;
q: out std_logic_vector(3 downto 0)
);
```

```

end reg;

architecture behavioral_reg of reg is
  component dff
  port(
    clk, reset, d : in std_logic;
    q : out std_logic
  );
  end component;

  signal reset: std_logic:= '0';
  begin

  dff0: dff
  port map (clk, reset, d(0), q(0));
  dff1: dff
  port map (clk, reset, d(1), q(1));
  dff2: dff
  port map (clk, reset, d(2), q(2));
  dff3: dff
  port map (clk, reset, d(3), q(3));

end behavioral_reg;

```

VHDL Testbench:

```

library ieee;
use ieee.std_logic_1164.all;

entity reg_tb is
end reg_tb;

architecture behavioral_reg_tb of reg_tb is
  component reg
  port(

```

```
d: in std_logic_vector(3 downto 0);
clk, clear: in std_logic;
q: out std_logic_vector(3 downto 0)
);
end component;
```

```
signal d, q: std_logic_vector(3 downto 0);
signal clk, clear: std_logic:= '0';
```

```
constant clk_period : time := 100 ns;
shared variable simend : boolean := false;
```

```
begin
 uut : reg port map (clk => clk,clear => clear, d => d, q => q);
```

```
clk_process :process
begin
while simend=false loop
clk <= not clk;
wait for clk_period/2;
end loop;
wait;
end process;
```

```
stim_proc: process
begin
d(0) <= '0'; d(1) <= '0'; d(2) <= '0'; d(3) <= '0';
wait for clk_period*2;
```

```

d(0) <= '0'; d(1) <= '1'; d(2) <= '0'; d(3) <= '1';
wait for clk_period*2;
clear <= '1';
d(0) <= '1'; d(1) <= '0'; d(2) <= '1'; d(3) <= '1';
wait for clk_period*2;
d(0) <= '0'; d(1) <= '0'; d(2) <= '1'; d(3) <= '1';
wait for clk_period*2;
simend := true;
wait;
end process;
end behavioral_reg_tb;

```

Output(4 bit Register):



Figure : Simulation output of 4-bit Register

T Flipflop:

VHDL Module:

```
library ieee;
use ieee.std_logic_1164.all;
entity TFF is
port( din: in std_logic;
      clk: in std_logic;
      rst: in std_logic;
      dout: out std_logic);
end TFF;
architecture behavioral of TFF is
begin
process(rst,clk,din)
begin
if (rst='1') then
dout<='0';
elsif(rising_edge(clk)) then
dout<=not din;
end if;
end process;
end behavioral;
```

VHDL Testbench:

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY TFF_tb IS
END TFF_tb;
COMPONENT TFF
PORT(
din : IN std_logic;
clk : IN std_logic;
rst : IN std_logic;
dout : OUT std_logic
);
END COMPONENT;
signal din : std_logic := '0';
signal clk : std_logic := '0';
signal rst : std_logic := '0';
signal dout : std_logic;
constant clk_period : time := 10 ns;
BEGIN
uut: TFF PORT MAP (
din => din,
clk => clk,
```

```

rst => rst,
dout => dout
);
clk_process :process
begin
clk <= '0';
wait for clk_period/2;
clk <= '1';
wait for clk_period/2;
end process;
stim_proc: process
begin
rst <= '1';
wait for 50 ns;
rst <= '0';
din <= '0';
wait for 50 ns;
rst <= '0';
din <= '1';
wait;
end process;
END;

```

Output(T flipflop):



Figure : Simulation Output of T flipflop

4 bit Shift Register:

VHDL Module:

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity Dflipflop is  
Port ( clk : in  STD_LOGIC;  
reset : in  STD_LOGIC;  
D : in  STD_LOGIC;  
Q : out  STD_LOGIC);  
end Dflipflop;
```

```
architecture struc of Dflipflop is  
signal qtemp: std_logic:= '0';  
begin  
Q<=qtemp;
```

```
process(clk,reset)  
begin
```

```
if(reset = '1')then  
qtemp<= '0';
```

```
elsif(rising_edge(clk))then  
if(D = '0')then
```

```
qtemp<= '0';  
else  
qtemp<= '1';  
end if;
```

```
else  
qtemp<=qtemp;  
end if;  
end process;  
end struc;  
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity shiftregister is  
Port ( clk : in  STD_LOGIC;
```

```

reset : in STD_LOGIC;
input: in std_logic;
Q : out STD_LOGIC_VECTOR(3 downto 0));
end shiftregister;

```

architecture Behavioral of shiftregister is

```

component Dflipflop
Port ( clk : in STD_LOGIC;
reset : in STD_LOGIC;
D : in STD_LOGIC;
Q : out STD_LOGIC);
end component;

```

```

signal C : std_logic_vector(2 downto 0);
begin
proc1:Dflipflop
port map(clk,reset,input,C(0));
Q(0)<= C(0);
proc2: Dflipflop
port map(clk,reset,C(0), C(1));
Q(1)<= C(1);

```

```

proc3:Dflipflop
port map(clk,reset,C(1),C(2));
Q(2)<= C(2);

```

```

proc4:Dflipflop
port map(clk,reset,C(2),Q(3));

```

end Behavioral;

VHDL Testbench:

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

```

```

ENTITY shiftregister_tb IS
END shiftregister_tb;

```

```

ARCHITECTURE behavior OF shiftregister_tb IS
COMPONENT shiftregister
PORT(

```



```
clk : IN std_logic;  
reset : IN std_logic;  
input : IN std_logic;  
Q : OUT std_logic_vector(3 downto 0)  
);  
END COMPONENT;
```

```
signal clk : std_logic := '0';  
signal reset : std_logic := '0';  
signal input : std_logic := '0';
```

```
signal Q : std_logic_vector(3 downto 0);
```

```
constant clk_period : time := 100 ns;  
shared variable simend: boolean:= false;
```

```
BEGIN
```

```
uut: shiftregister PORT MAP (  
clk => clk,  
reset => reset,  
input => input,  
Q => Q  
);
```

```
clk_process :process  
begin  
while simend= false loop  
clk<=not clk;  
wait for clk_period/2;  
end loop;  
wait;  
end process;
```

```
stim_proc: process  
begin
```

```
input <= '0';  
wait for clk_period;  
input<='1';  
wait for clk_period;  
input <= '0';  
wait for clk_period;
```

```

input <= '1';
wait for clk_period;
input <= '1';
wait for clk_period;
input <= '0';
wait for clk_period;
simend :=true;

```

```

wait;
end process;

```

```

END;

```

Output(4 bit Shift Register):



Figure : Simulation output of 4-bit Shift Register

5. 4-Bit Counter :

VHDL module :

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity UPDOWN_COUNTER is
Port ( clk: in std_logic; -- clock input
reset: in std_logic; -- reset input
up_down: in std_logic; -- up or down
counter: out std_logic_vector(3 downto 0) -- output 4-bit counter
);
end UPDOWN_COUNTER;
architecture Behavioral of UPDOWN_COUNTER is
signal counter_updown: std_logic_vector(3 downto 0);
begin
process(clk,reset)
begin
if(rising_edge(clk)) then
if(reset='1') then
counter_updown <= x"0";
elsif(up_down='1') then
counter_updown <= counter_updown - x"1"; -- count down
else
counter_updown <= counter_updown + x"1"; -- count up
end if;
end if;
end process;
counter <= counter_updown;
end Behavioral;
```

VHDLTestbench :

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity tb_counters is
end tb_counters;
architecture Behavioral of tb_counters is
component UPDOWN_COUNTER
Port ( clk: in std_logic; -- clock input
reset: in std_logic; -- reset input
up_down: in std_logic;
counter: out std_logic_vector(3 downto 0) -- output 4-bit counter
);
end component;
signal reset,clk,up_down: std_logic;
signal counter:std_logic_vector(3 downto 0);
```

```

begin
dut: UPDOWN_COUNTER port map (clk => clk, reset=>reset, up_down => up_down, counter
=> counter);
clock_process :process
begin
clk <= '0';
wait for 10 ns;
clk <= '1';
wait for 10 ns;
end process;
stim_proc: process
begin
reset <= '1';
up_down <= '0';
wait for 20 ns;
reset <= '0';
wait for 300 ns;
up_down <= '1';
wait;
end process;
end Behavioral;

```

Output(4 bit counter):

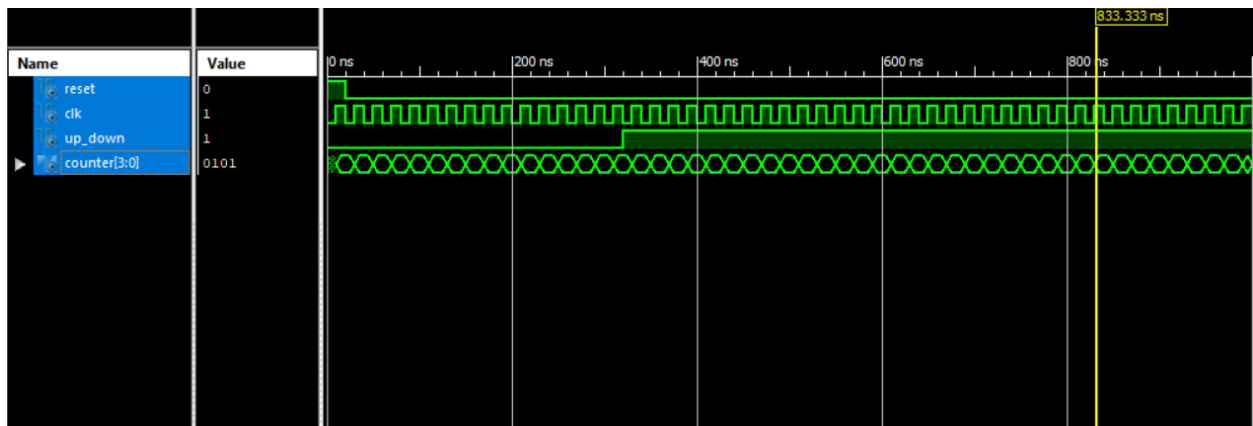


Figure : Simulation output of 4-bit counter